



UNIVERSITY OF ENERGY AND NATURAL RESOURCES, SUNYANI, GHANA
SCHOOL OF ENGINEERING
DEPARTMENT OF COMPUTER AND ELECTRICAL ENGINEERING
Level 300: First Semester Examinations 2019/2020
Bachelor of Science (Computer Engineering, Electrical & Electronic Engineering)
ELNG 303: LINEAR ELECTRONIC CIRCUITS
DECEMBER, 2019 *MDK* Time: 2½ hours

INSTRUCTIONS: ANSWER ALL FOUR QUESTIONS)

Question One [3+(2+4)+4=13]

- a) With the aid of diagrams, briefly describe the process of photolithography used in the fabrication of monolithic ICs.
- b) A circuit is built around a bi-polar NPN transistor. The base network has a diode and a capacitor in series while the collector is connected to a power supply through a resistor. If the emitter is connected to ground:
- Draw the circuit
 - Provide all the masking layout of the circuit
- c) Fig1.1 shows a p-diffusion resistor fabricated with a sheet resistance of 120 Ohm per square. The corners and the pads are estimated to have 0.6 of the value of a regular sheet resistance. Find the value of the resulting resistor.

 


Fig1.1

- * Infinite input impedance
- * Infinite bandwidth
- * Zero output impedance
- * Infinite open-loop voltage gain
- * Infinite common-mode rejection ratio

Question Two [2+4+6+6=18]

- Mention the characteristics of an ideal op-amp.
- Draw a shunt regulator and clearly show the four main elements. Derive an expression for the output voltage.
- A differential amplifier has an output voltage given by $V_o = 9V_1 - 10V_2$. The two inputs are $V_1 = 10\text{ mV}$ and $V_2 = 20\text{ mV}$. Determine common mode input voltage, common mode gain and the differential gain.
- In Op-Amp circuit of Fig. 2.1, find V_o in terms of V_1 and V_2 assume the ideal op amp model. Find an expression for V_o . If $V_1 = 1.5\text{V}$ and $V_2 = 3.0\text{V}$, find V_o for $R_1 = 1\text{k}\Omega$ and $R_2 = 2\text{k}\Omega$

 


Fig 2.1

Question Three [2+4+(2x3)=12]

- State and explain the various classifications of power amplifiers.
- For a class B power amplifier, show that the maximum efficiency is 78.5%.
- For a class B amplifier providing a 20V peak-to-peak signal to an 8Ω speaker and a power supply of $V_{cc} = 15\text{V}$, determine:
 - Input power
 - Output power
 - Circuit efficiency

$$\text{Max. } \eta = \frac{V_o V_m}{4V_{cc}}$$

$$\eta = \frac{V_o V_m}{4V_{cc}}$$

$$\eta = 78.5\%$$

$$P_{dc} = \frac{2V_{cc} I_E}{\pi}$$

$$P_{o(ac)} = \frac{V_m^2}{2R_L}$$

$$\eta = \frac{P_{o(ac)}}{P_{dc}} \times 100\%$$

Question Four [4+4+(3x3)=17]

Consider the common-emitter BJT amplifier circuit shown in Figure 4.1. Take $\beta_1 = \beta_2 = 200$, $V_{BE} = 0.7V$ and thermal voltage as $26V$. Answer the following questions.

- (a) Determine the emitter current I_{E2} , I_{E1} and hence r_{e2} and r_{e1}
- (b) Draw the AC equivalent circuit and determine:
 - i) Input impedance, Z_1 , Z_2 and Z_{in}
 - ii) Gain of the transistor, A_{v2} and A_{v1}
 - iii) Output voltage gain with signal, A_{vs}

 


Fig. 4.1

UNIVERSITY OF ENERGY AND NATURAL RESOURCES, SUNYANI, GHANA
SCHOOL OF ENGINEERING



DEPARTMENT OF COMPUTER AND ELECTRICAL ENGINEERING

Level 300: End of Semester Examinations 2021/2022

Bachelor of Science (Computer, Electrical & Electronic Engineering)

ELNG 303: LINEAR ELECTRONIC CIRCUITS

May/June, 2022

Time: 2½ hours

Material required: Class material (To be brought in by students)

INSTRUCTIONS: ANSWER ALL QUESTIONS

Question 1 (12 Marks)

- (a) State and explain briefly the five planar processes in the fabrication of monolithic IC
- State the main difference between negative and positive photoresist and at what condition each is applied
 - State the significance of passivation in IC fabrication and the material used.
- (b) Provide a step-by-step masking levels for the fabrication of a **NPN** Transistor indicating the type of photo-resist used.

Question 2 (20 Marks)

The two-stage amplifier shown in Fig. 2 is designed with a *FET*, *TR1* and silicon *BJT*, *Q1* with the manufacturer's specifications for β (*Q1*) at 25°C as 150 and g_m (*TR1*) as 3500 μS . Given $R_g = 1.5 k\Omega$, $R_1 = 6 M\Omega$, $R_2 = 4 M\Omega$, $R_d = 2.4 k\Omega$, $R_s = 500 \Omega$, $R_3 = 15 k\Omega$, $R_4 = 4.7 k\Omega$, $R_c = 2.7 k\Omega$, $R_e = 470 \Omega$, $R_L = 2.2 k\Omega$ and supply voltage as 20V. Using the Fig.2 and component values given, answer the following questions.

Calculate:

- Draw the small signal equivalent circuit using the model treated in class
- Emitter current I_E
- Emitter resistance r_e
- Voltage gain at stage 2 (*BJT*), A_{v2}
- Calculate input impedance of the second stage (*BJT*), Z_2
- Calculate the gain of the first stage (*FET*), A_{v1}
- Calculate the input impedance of the first stage Z_1
- Calculate the overall gain with signal, A_{vs}
- If V_s is a sinusoidal voltage of $5mV \cos \omega t$, what will the output voltage be?
- On the same graph plot the input and output voltage against ωt .

 


Fig. 2

Question 3 (16 Marks)

- State and explain the different between Class A and Class B power amplifiers.
- How do you minimize the effect of crossover distortion in class B power amplifier?
- A class A power amplifier is supplied with 20V and biased to operate at a quiescent base current of 19.3mA with a base peak current of 10mA and a collector load of 20 Ω . Given that $\beta=25$, Calculate the amplifier:
 - Input power, $P_{i(dc)}$
 - Output power, $P_{o(ac)}$
 - Efficiency, η
- A complementary push-pull amplifier has to deliver 2.5 W into a load of 8 Ω . Determine:
 - The maximum power dissipation required for each transistor;
 - The supply voltage required;
 - The peak load current.

Question 4 (12 Marks)

- State five characteristics of an ideal op-amp.
- For the difference amplifier shown in Fig. 4.1, find an expression for the output voltage V_o . Evaluate V_o if $R_1 = 10k\Omega$, $R_2 = R_3 = 15k\Omega$ and $R_f = 20k\Omega$.
- Evaluate the gain.

 


Fig. 4.1



UNIVERSITY OF ENERGY AND NATURAL RESOURCES, SUNYANI, GHANA
SCHOOL OF ENGINEERING

DEPARTMENT OF COMPUTER AND ELECTRICAL ENGINEERING

Level 300: First Semester Examinations 2020/2021

Bachelor of Science (Computer Engineering, Electrical & Electronic Engineering)

ELNG 303: LINEAR ELECTRONIC CIRCUITS

April, 2021

Time: 2½ hours

Material required: Class material (To be brought in by students)

INSTRUCTIONS: ANSWER ALL QUESTIONS (each question carries 15 marks)

Question 1

(a) The following processes are used in the fabrication of monolithic ICs, explain each of them in detail:

- Oxidation
- Diffusion
- Epitaxy
- Photolithography
- Thin Film Deposition

(b) Using the list in (a) provide a step-by-step masking levels of the fabrication of NPN transistor indicating the type of photo-resist used.

Question 2

The two-stage amplifier shown in Fig. 2 is designed with a FET, TR1 and silicon BJT, Q1. The manufacturer's specifications for β (Q1) at 25°C as 150 and g_m (TR1) as 3500 μS . Given $R_g = 1.5 k\Omega$, $R_1 = 6 M\Omega$, $R_2 = 4 M\Omega$, $R_d = 2.4 k\Omega$, $R_s = 500 \Omega$, $R_3 = 15 k\Omega$, $R_4 = 4.7 k\Omega$, $R_5 = 2.7 k\Omega$, $R_e = 470 \Omega$, $R_L = 2.2 k\Omega$ and supply voltage as 20V. Using the Fig. 2 and component values given, answer the following questions.

Calculate:

- Emitter current I_E
- Emitter resistance r_e
- Voltage gain at stage 2, A_{v2}
- Calculate input impedance of the second stage, Z_2
- Calculate the gain of the first stage, A_{v1}
- Calculate the input impedance of the first stage Z_1
- Calculate the overall gain, A
- If v_g is a sinusoidal voltage of $5mV \cos \omega t$, what will the output voltage be?



UNIVERSITY OF ENERGY AND NATURAL RESOURCES, SUNYANI, GHANA
SCHOOL OF ENGINEERING
DEPARTMENT OF COMPUTER AND ELECTRICAL ENGINEERING
Level 300 Mid-Semester Examinations 2021/2022
Bachelor of Science (Computer, Electrical and Electronic Engineering)

ELNG 303: LINEAR ELECTRONIC CIRCUITS
April, 2022
Time: 1 hour

Attempt all questions

Question 1

(a) Briefly explain the following terms as applied to IC fabrication

- (i) Epitaxial Growth
- (ii) Photolithography
- (iii) Thin film deposition

(b) A circuit is built around a bi-polar NPN transistor. The base network has a diode and a capacitor in series while the collector is connected to a power supply through a resistor. If the emitter is connected to ground:

- i) Draw the circuit
- ii) Provide all the masking layout of the circuit.

Question 2

Given the circuit diagram of Fig. 2 with $V_{CC} = 12V$, and $\beta = 52$.

(a) Using the re model; draw the small signal equivalent circuit.

(b) Determine:

- (i) The gain of the transistor.
- (ii) The input impedance of the transistor.
- (iii) The overall gain of the amplifier.

 


Fig. 2